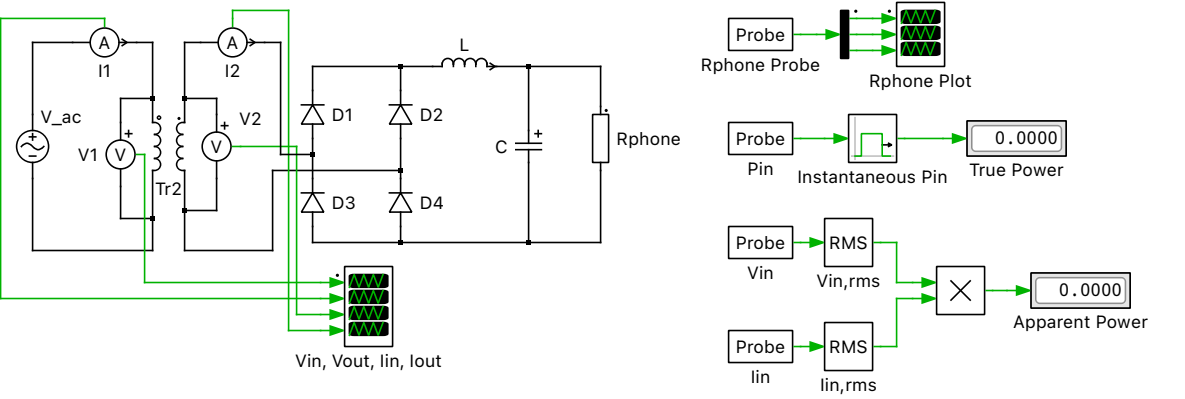


Iphone Charger Rectifier Analysis



- Specs to meet:
1. Wall outlet voltage: 120 Vrms
 2. Converter Average Output Voltage: 5V
 3. Average Power: 5W
 4. Grid Frequency: 60 Hz
 5. Voltage ripple under 1%

- Analysis Components
1. Identify THD with cursors
 2. Calculate power factor with $P_{true}/P_{apparent}$

Note: Run simulation through steady state analysis tool found under "Simulation" -> "Analysis Tools" -> "Steady-State Analysis"

Operating settings: Periodic, auto, 0 seconds, 100 cycles